

Bob Pease  
Lab notes 2005





What's All This

- Common

Mode

Rejection

Stuff?

(Anyhow....)

/RAP



PART I: HISTORY....  
R.A. PEASE....

PART II -  
- How to test Op amps  
for CMRR

---


PART III  
DESIGN FOR RAIL-TO-RAIL  
CM Range

---

Part IV CIRCUIT DESIGN  
FOR GOOD CMRR




ONCE UPON A TIME....

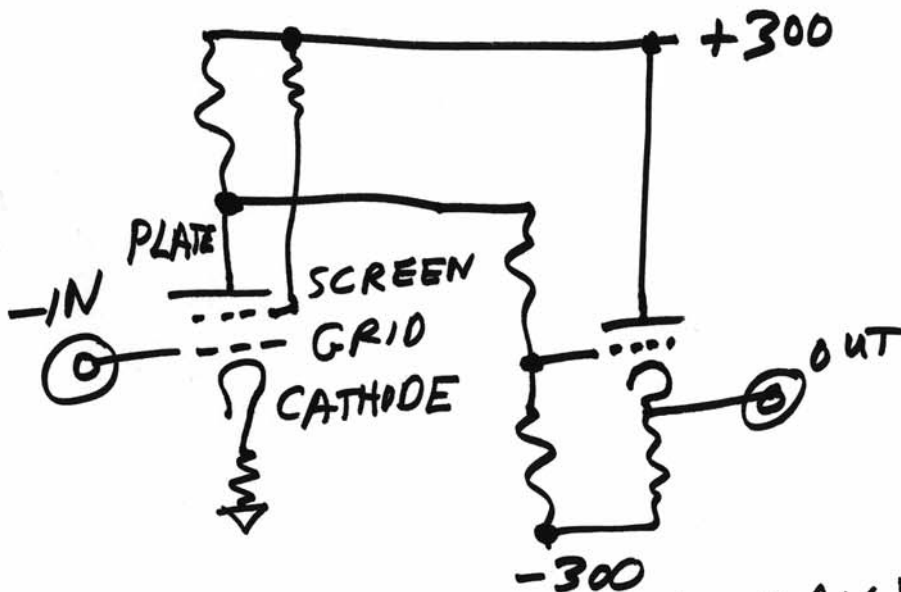

- OP AMPS DIDN'T HAVE  
ANY COMMON MODE RANGE....

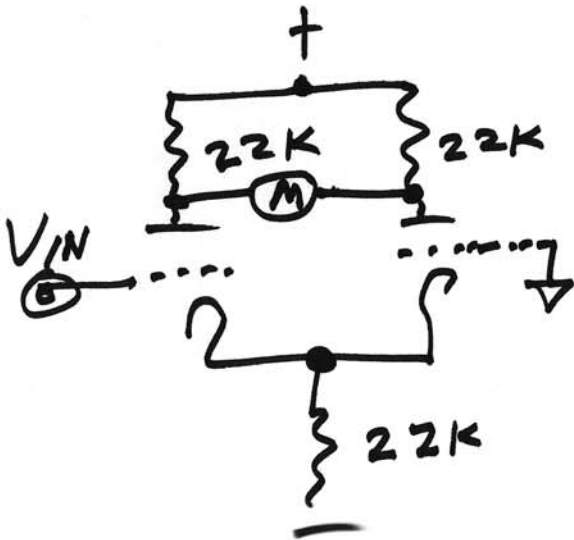
YES, DIFFERENTIAL AMPLIFIERS  
WERE INVENTED IN THE  
1920'S...



RAP




AND THE K2-W CAME  
ALONG ~ 1952

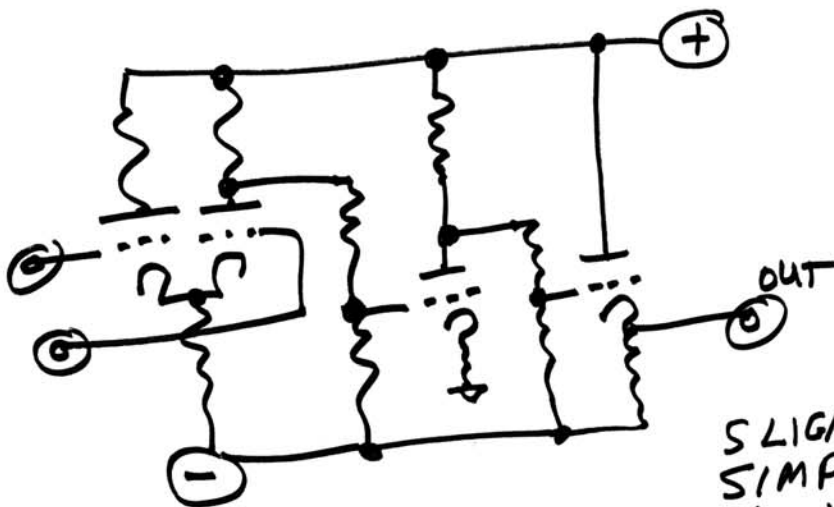

SLIGHTLY  
SIMPLIFIED ...  
...  $\frac{1}{2}$  = 1/2 12AX7


CMRR  $\approx$  300 for  $\pm 50V$

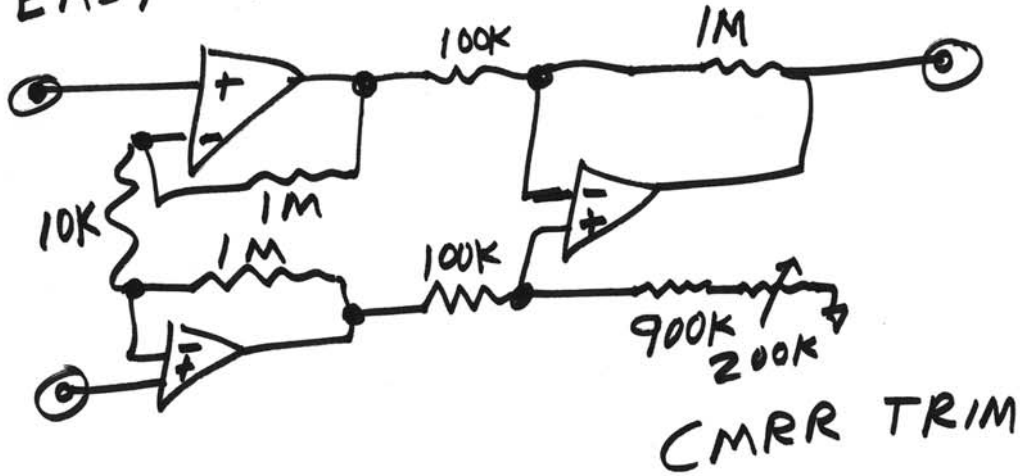STILL - Differential Amplifier  
CIRCUITS WERE NOT  
EASY TO DESIGN WITH TUBES...



[VOS TRIM NOT SHOWN]

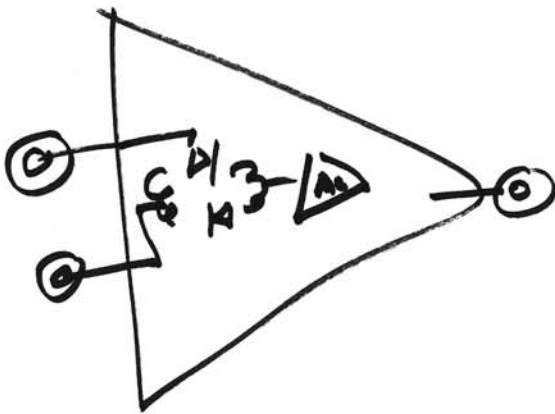
THE PHILBRICK P2 USED  
8 GERMANIUM TRANSISTORS TO  
PROVIDE A  $\pm 200$  VOLT  
CM RANGE



THE CMRR WAS  $\sim \infty$   
- IN 1961....


BOB

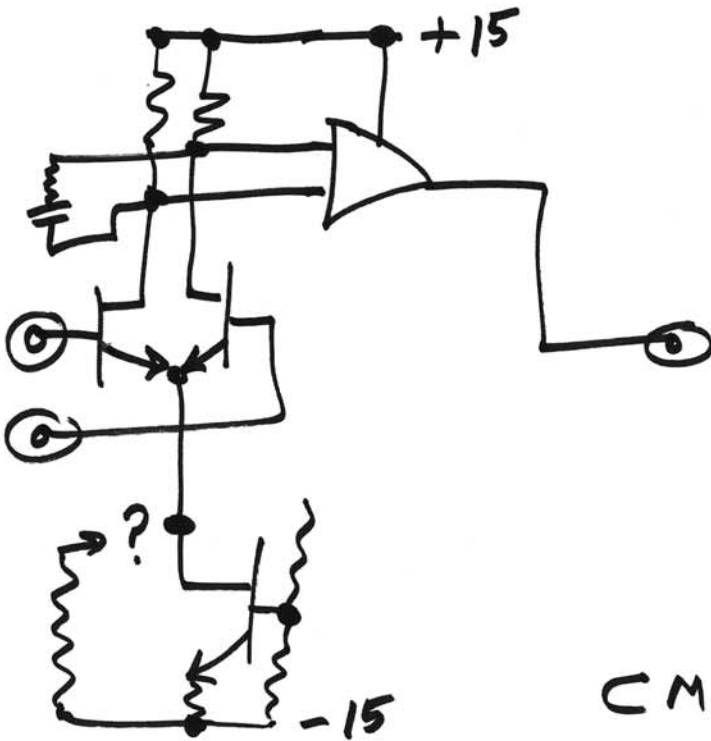SILICON TRANSISTORS  
MADE GOOD OP-AMPS  
POSSIBLE




CMRR > 10,000 WITH  
GOOD MATCHED NPN'S....

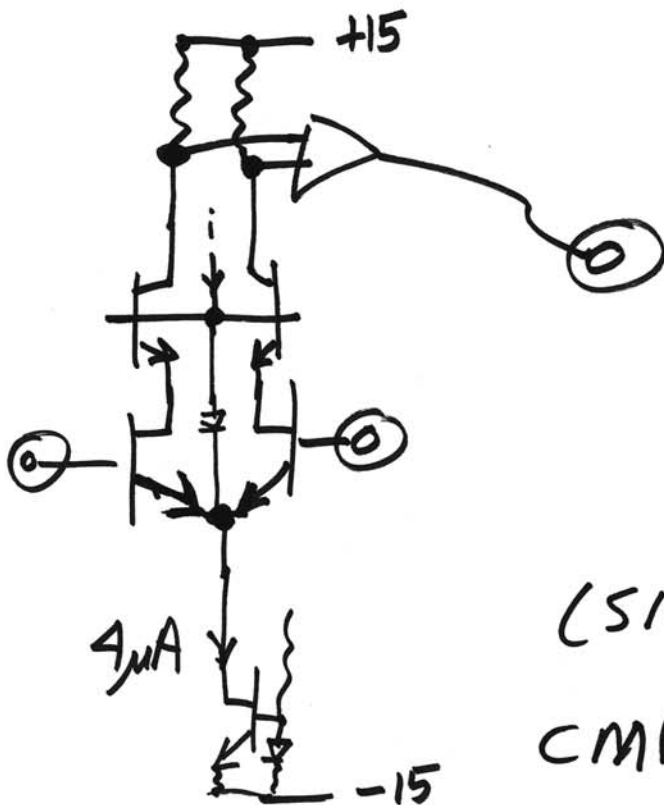BOB WIDLAR'S LM108  
MADE HIGH CMRR  
FEASIBLE




(SIMPLIFIED CIRCUIT)  
CMRR = 100,000  
TYP.

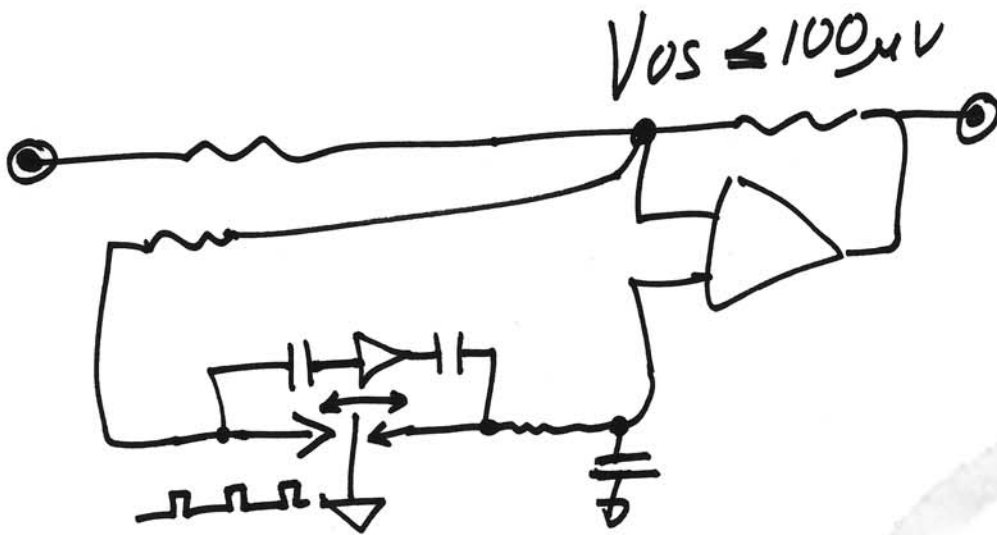CHOPPER-STABILIZED  
AMPLIFIERS USED TO GIVE  
LOW OFFSET - BUT ONLY AT  
GROUND



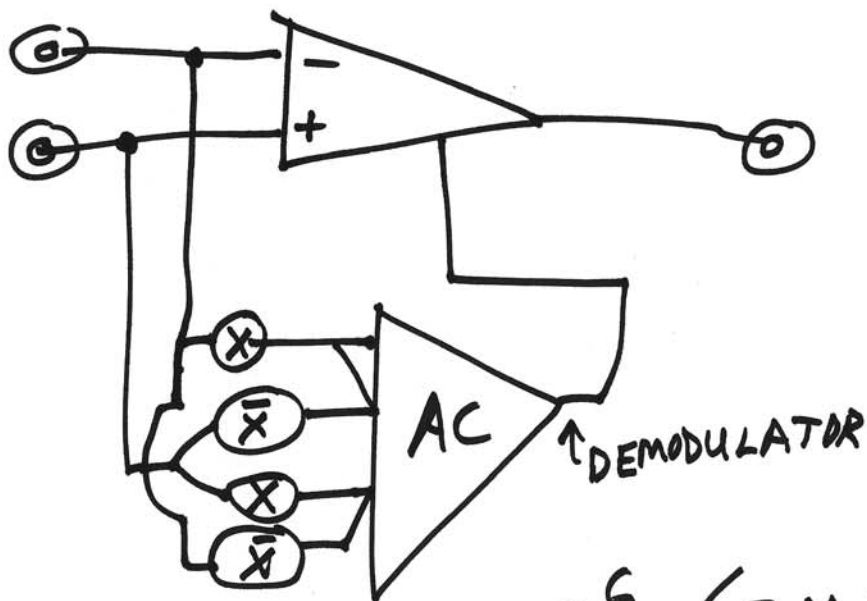CMOS CHOPPERS MAKE  
GOOD CMRR FEASIBLE UP TO  
+ 2.7V



CMRR  $> 10^6$  (3M typical)





WHAT'S ALL THIS

COMMON

MODE

REJECTION  
STUFF?


(ANYHOW.....?)

PART II:

HOW TO MEASURE


OP-AMP CMRR....

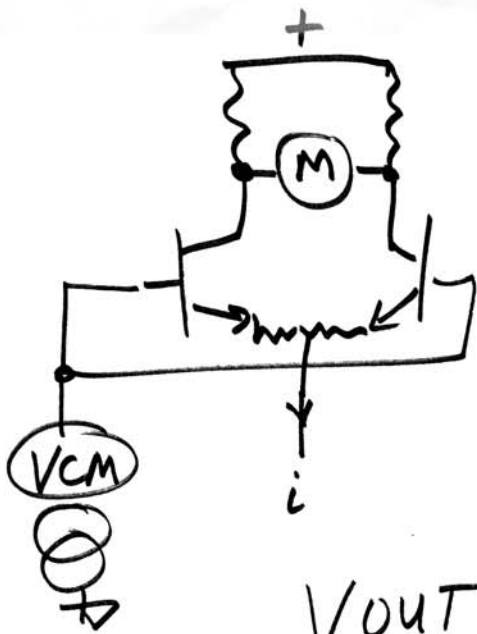OK - NOW WE HAVE GOOD  
OP-AMPS - HOW TO MEASURE?




$V_{OUT} = A_V \times V_{CM} / CMRR$   
BUT THIS ONLY WORKS FOR  
LOW GAIN - NOT FOR  
OPAMPS...

IS THIS A GOOD WAY TO MEASURE CMRR?

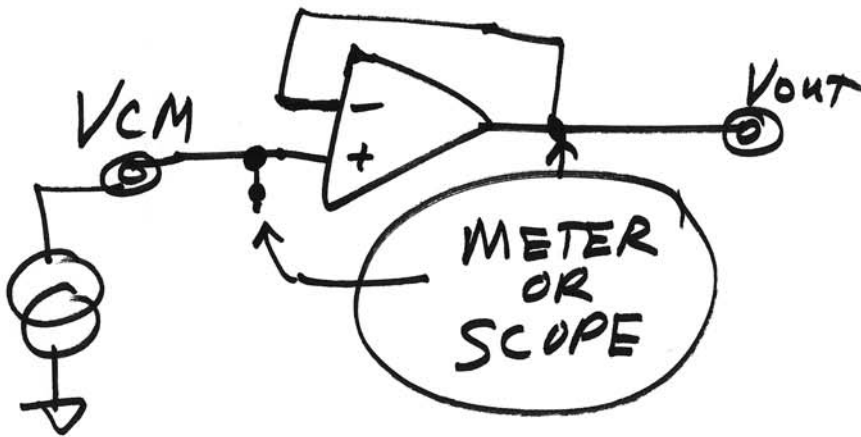


- NO -

RAP

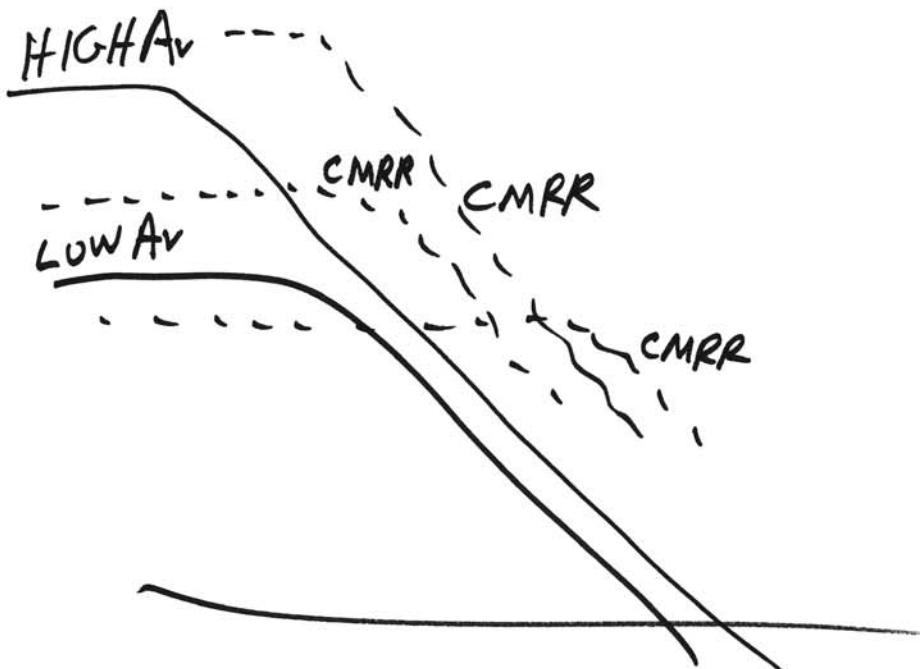


IN GENERAL - YOU CAN'T PREDICT  
 HIGH OR LOW DC GAIN OR CMRR,  
 HIGH OR LOW AC GAIN OR CMRR.

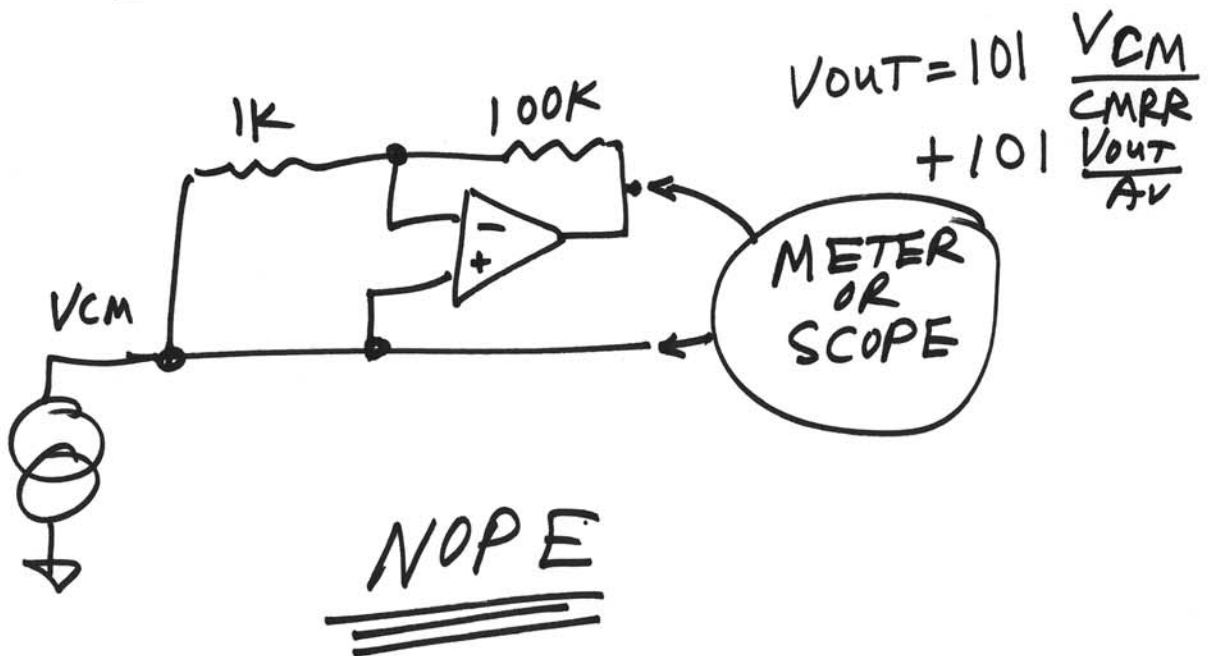AH - THIS MUST BE A  
GOOD WAY TO MEASURE CMRR



THIS HAS TO BE GOOD

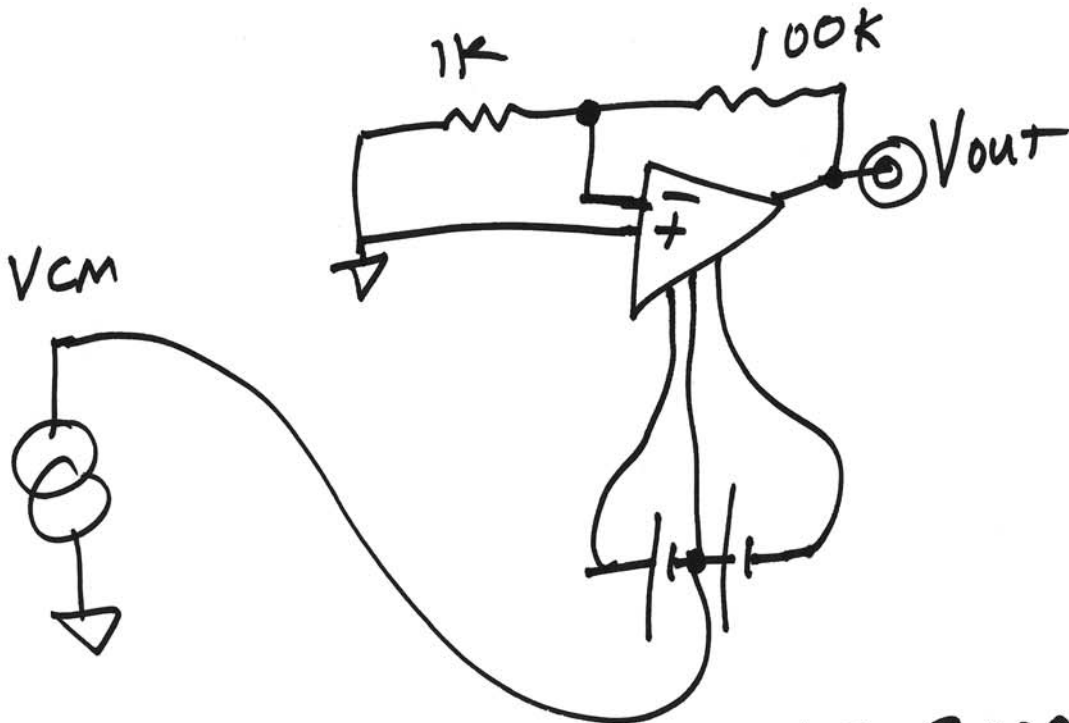


U.H. - U.H. NOT GOOD

$$V_{out} = 101 [V_{cm} / CMRR + V_{out} / A_v]$$


RAP 2005

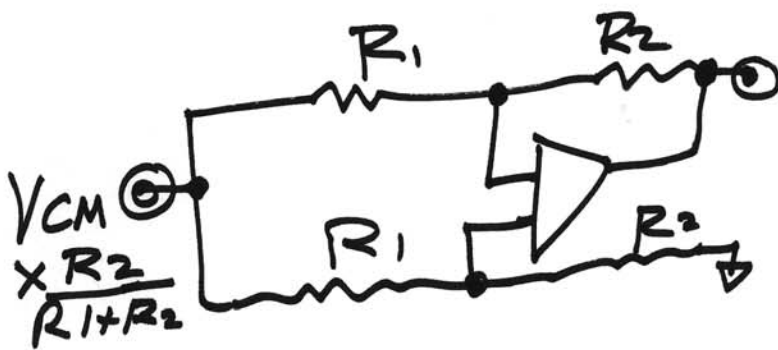OK, HOW ABOUT THIS?  
- ASSUME PERFECT RESISTORS



- THIS IS GOOD - NOW -  
WHERE DO WE GET THE  
"PERFECT R'S" ??

AHA - WE'VE GOT IT!!

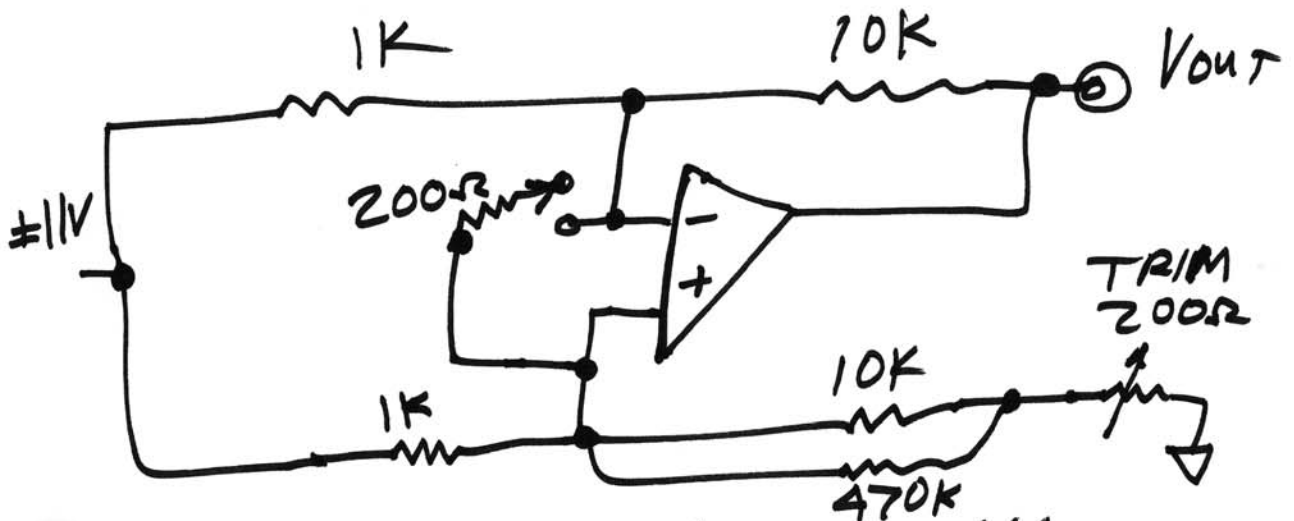

$$\text{NOISE GAIN} = 11 \text{ - or - } 111$$


$$\text{So } V_{out} (p-p) = (V_{cm}/CMRR) \times 11 \text{ or } 111$$

$$\text{THUS - } V_{cm}/CMRR \times 100 = \Delta V_{out}$$



WHAT IF YOU NEED TO  
MEASURE CMRR > 110dB?


EASY!

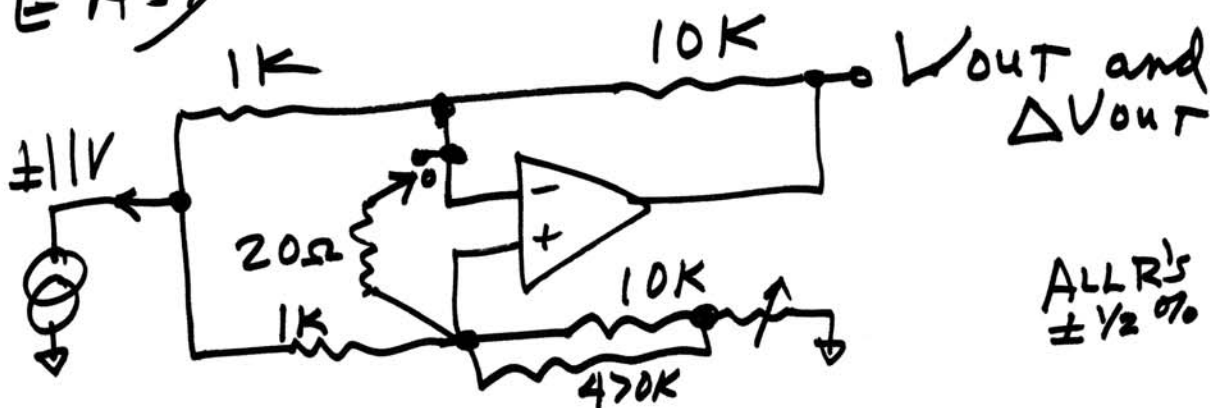

NOISE GAIN = 11 or 1011

SO  $\Delta V_{out} = [V_{CM} / CMRR] \times 1000$

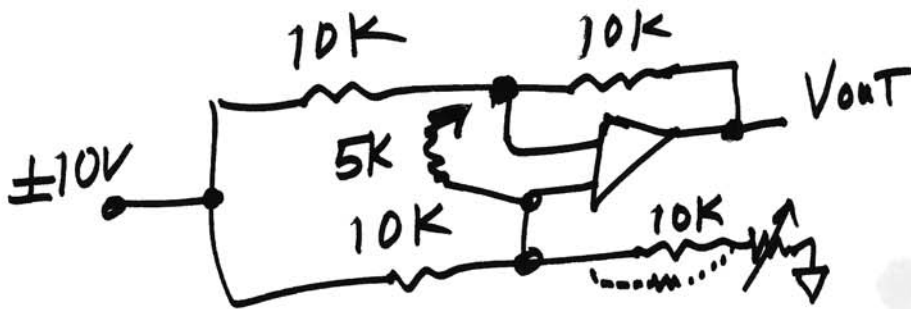WHAT IF YOU NEED  
TO MEASURE CMRR  
FOR 50KHz?



$$NG = 2 \text{ or } G$$


$$A \times V_{CM} / CMRR = \Delta V_{OUT}$$

$$BW \approx GBW / 10$$


CAUTION!  
DC CMRR

Ac CMRR

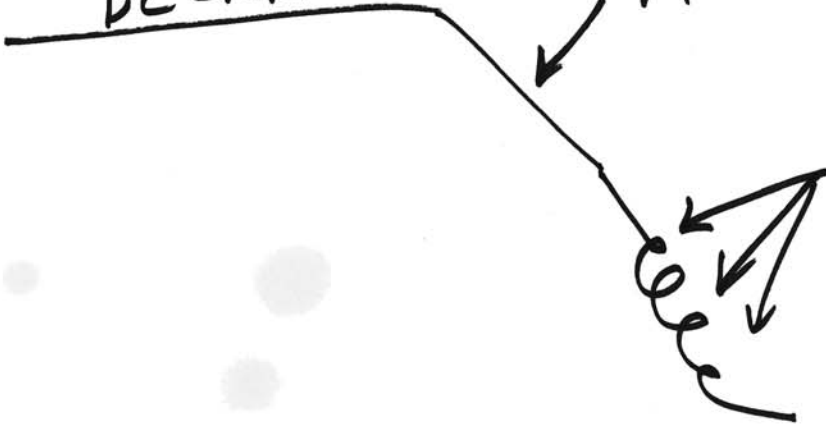NONLINEAR  
ERROR  
DUE TO  
CM  
SLEW  
LIMIT



ANOTHER VALID WAY  
TO MEASURE CMRR:

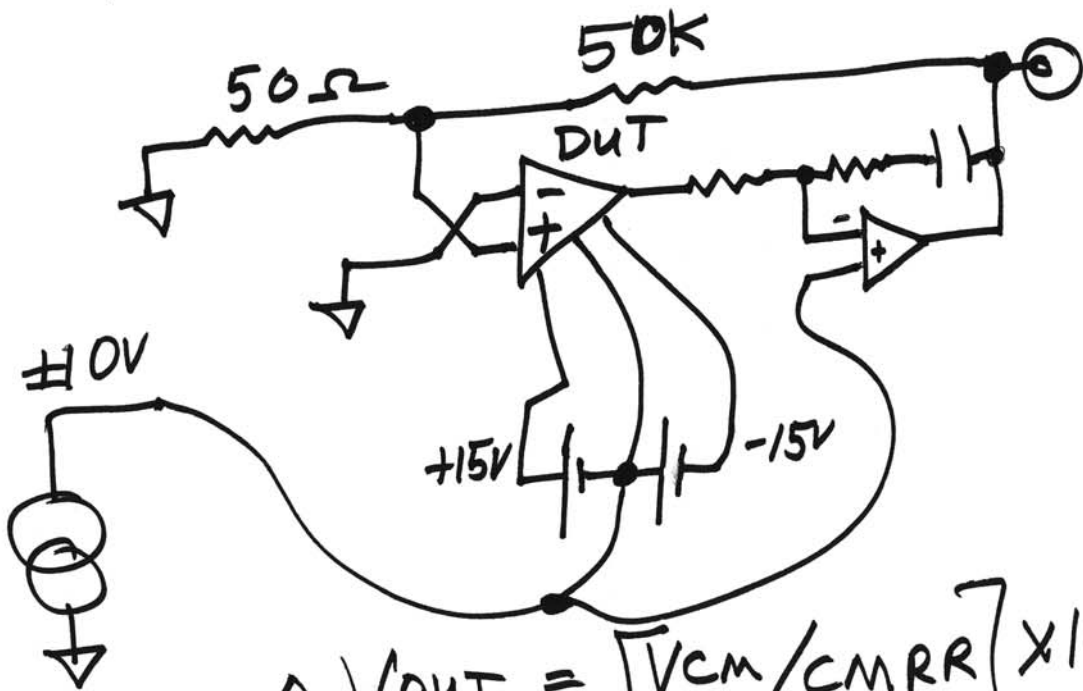

$$\Delta V_{out} = \left[ \frac{V_{cm}}{CMRR} \right] \times 1000$$

BUT,  
BEWARE, THIS WORKS  
ONLY AT DC & VERY  
LOW FREQUENCIES.

- AC ERRORS ARE -
- UNSPECIFIED.

/RAP



What's All This

COMMON  
MODE

REJECTION

STUFF?

(Anyhow.....)

Part III -  
Rail-to-Rail  
CM Range

RAP





LIST OF TYPICAL  
OP-AMPS WITHOUT  
+Vs OR -Vs Rail CM Range

- LM741
- LM725
- LM108
- LM709 - and -
- MANY MANY MORE....

LIST OF OPAMPS WITH  
CM RANGE TO  $-V_S$   
[GROUND]

- LM 358 - LM 324
- LMV324 - LMV322 - LMV321
- LMC 660 - (QUAD) LMC 662 (DUAL)
- MANY MORE -
- PLUS - ALL RAIL-TO-RAIL -  
INPUT CIRCUITS


LIST OF OP AMPS  
WITH CM RANGE TO  $+V_S$  -

- LM101A - LM301A
- LF156 - 356
- LF411 - LFA12 (DUAL)
- LF347, LF ~~44~~
- LF351, LF 353

- AND - OF COURSE -  
ALL RAIL-TO-RAIL INPUT  
AMPLIFIERS


# HOW TO MAKE - A - RAIL-TO-RAIL INPUT AMPL

① Pump it up - (+5V)

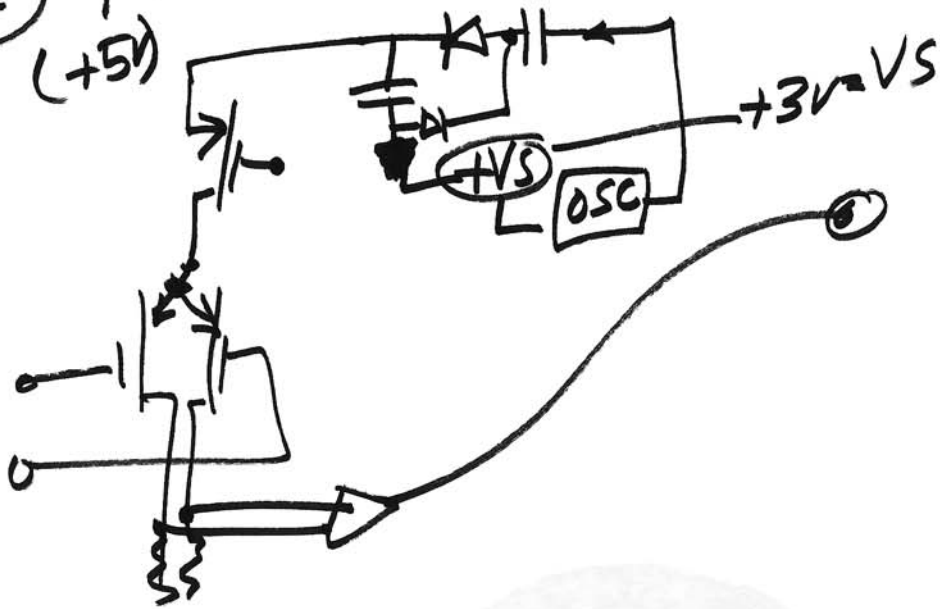


MAKE A R-R INPUT USING

② 2 INPUTS

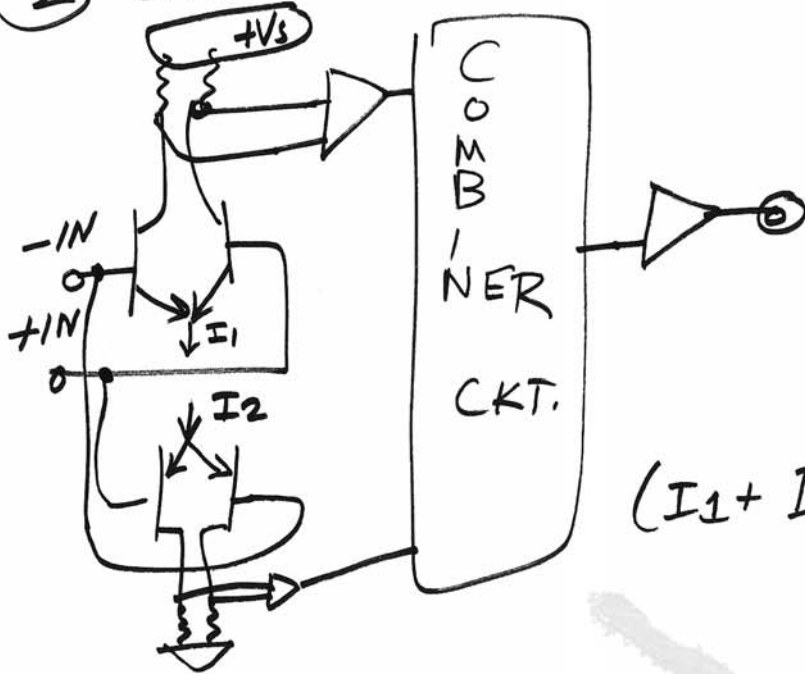

$$(I_1 + I_2 \approx \text{CONSTANT})$$

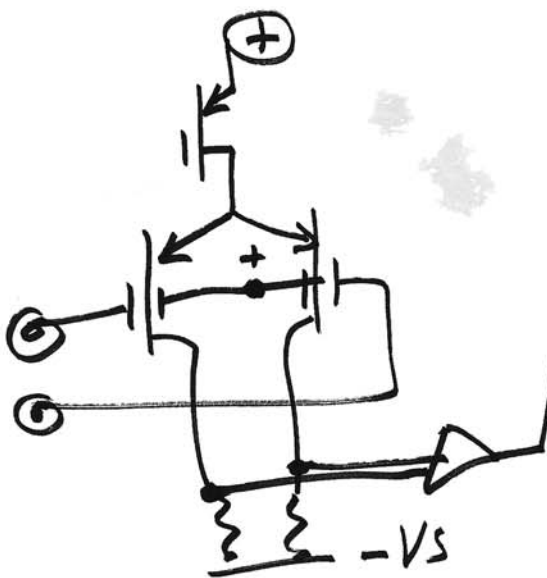
# HOW TO MAKE R-R $V_{cm}$ AMPLIFIERS SWEEPING USING MOS-FETS (U.S. PAT. ...)



- ### ADVANTAGES -
- VERY LINEAR
  - LOW NOISE
  - HIGH  $Z_{in}$

HOW TO MAKE HIGH CM Range...

④ USE TRANSFORMERS...

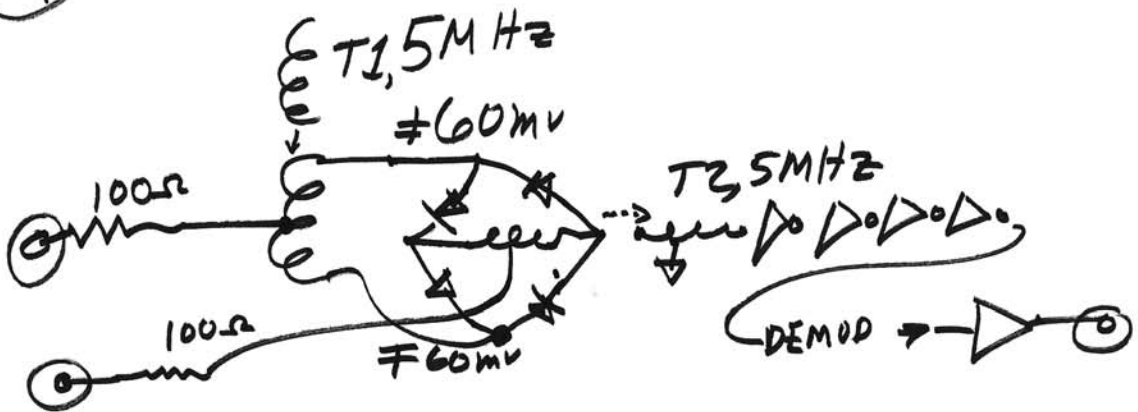

- ADVANTAGES -
- $V_{CM} > 100V$
  - $Z_{IN} > 100M\Omega$
  - $L_{NOISE} - 1\mu V$  for  $100Hz$

LATER WE'LL  
EXPLAIN WHY  
YOU MAY (OR MAY NOT)  
NEED RAIL-TO-RAIL  
C.M. RANGE

RAP

/more later. RAP



WHAT'S ALL THIS

CMRR  
STUFF, ?


(Anyhow?)

(PART III)

RAP 2005

# Differential Amplifiers


OR Instrumentation Amplifiers.

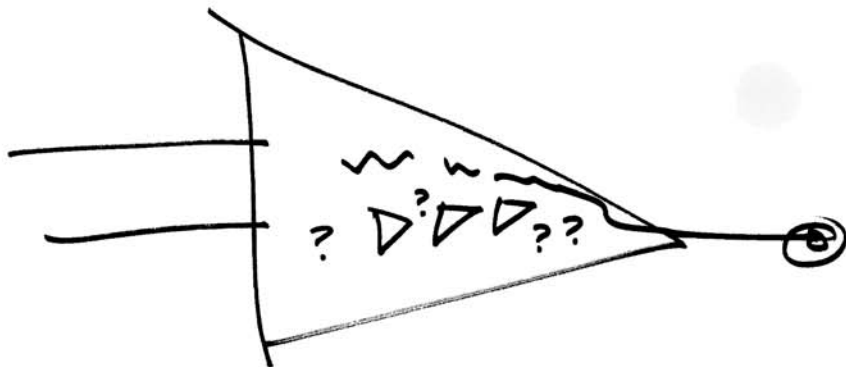


OK - WHAT IS  
AN "INSTRUMENTATION  
Amplifier"?

RAP

GAIN = K

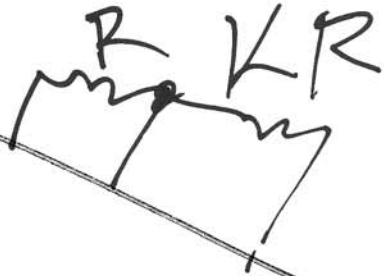

$Z_{IN} = \text{HIGH}$

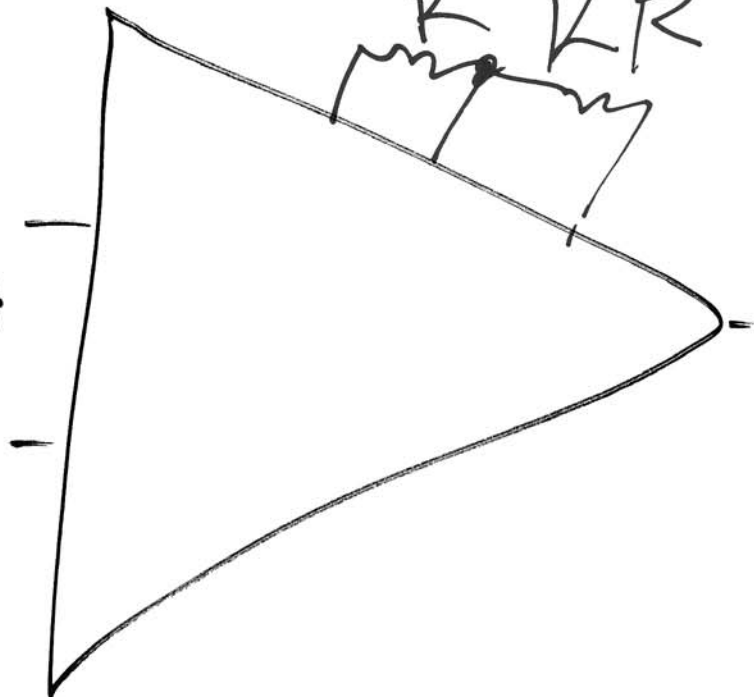


NOTE, THE OLD  
MA725 data-sheet  
SAID IT WAS "AN  
INSTRUMENTATION  
AMPLIFIER"


It wasn't....

It isn't....

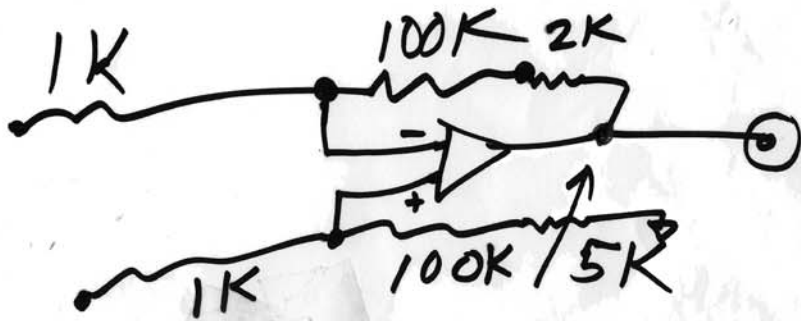
NOTE -  
(almost) ALL  
Instrumentation Amplifiers  
need R TRIMS....



You'll need a TRIM POT.  
for CMRR

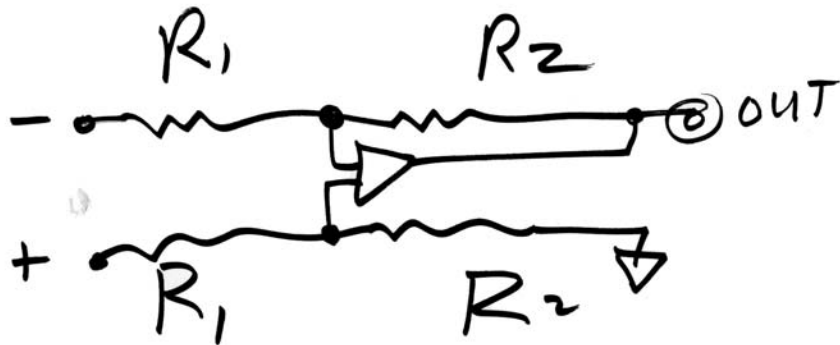

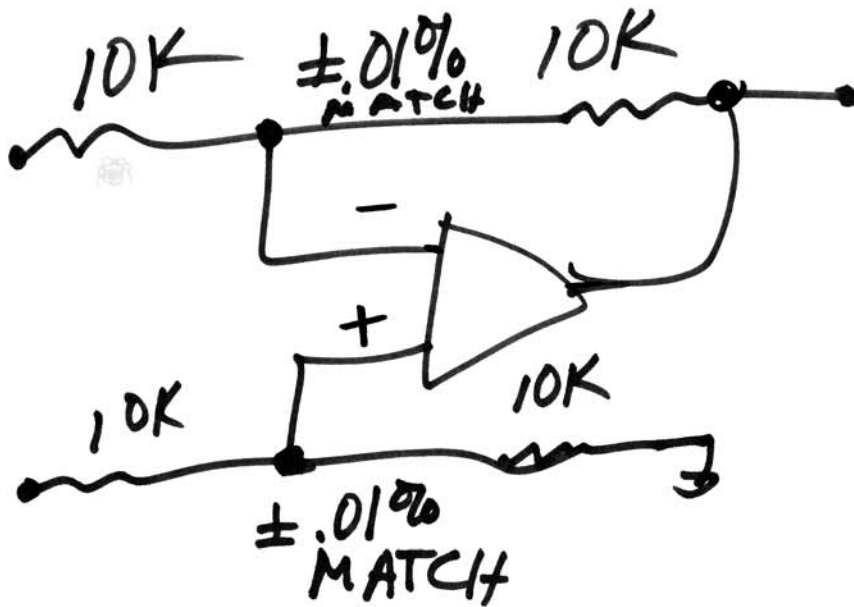- GOOD Differential Amplifier
- Needs TRIMS
- BUT -  $Z_{IN}$  ISN'T HIGH.....



YOU WANT  
THIN-FILM  
NETWORKS WITH  
 $0.01\%$  MATCHING....



NOT JUST FOR  
CORRECTING  
(CANCELLING OUT)  
the OP-amp's CMRR


BUT R-RATIO

1% Resistors? Ha!

0.1% Resistors? (A BIT  
BETTER.)

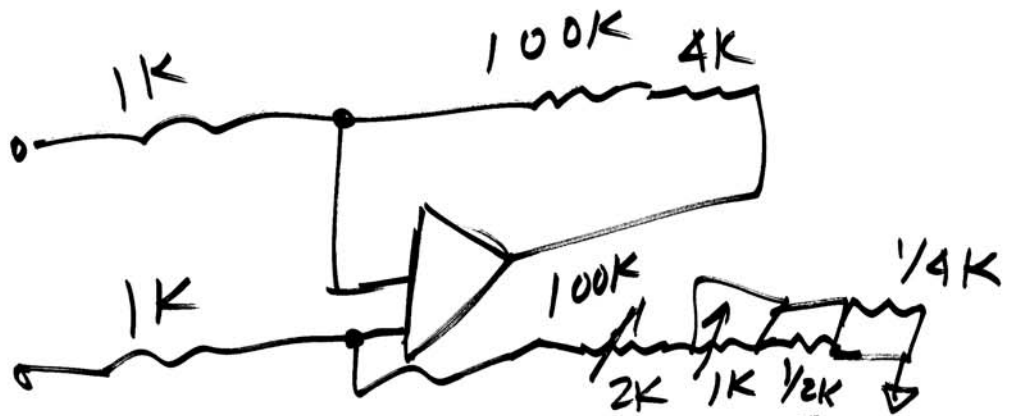
0.01% MATCH? .....

DO YOU WANT TO TRIM  
YOUR CMRR  
WITHOUT A POT?




Refer to LB-46...

# EXAMPLE ...

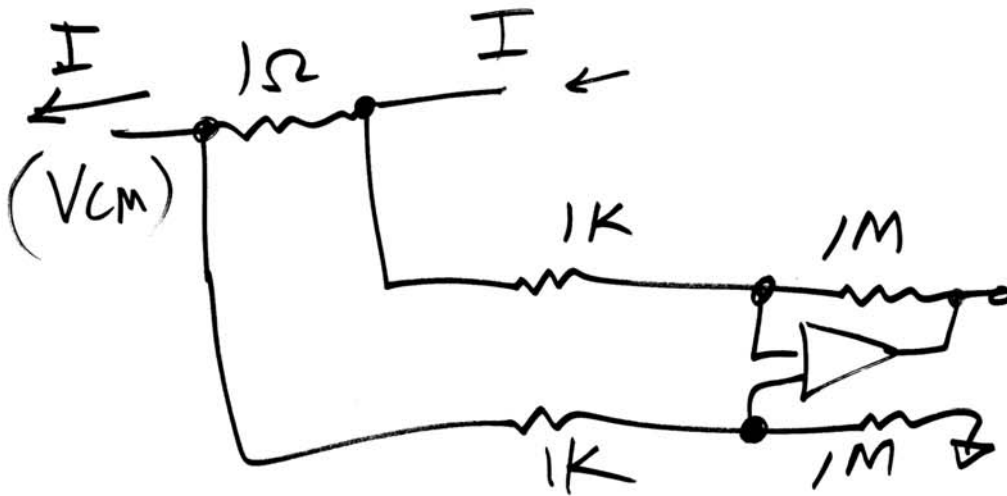


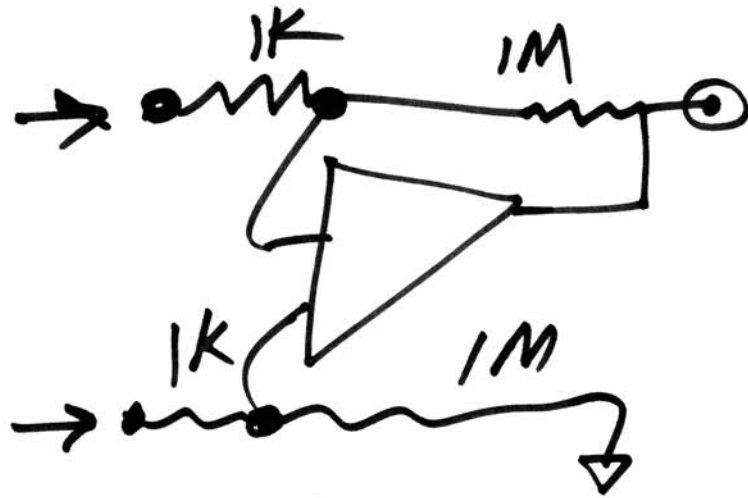Beware of -  
-  $V_{OS}$  -  
- CMRR .....




OK —  
What is the  $Z_{IN}$ ?  
1K?  
1M?

IMPROVED!!

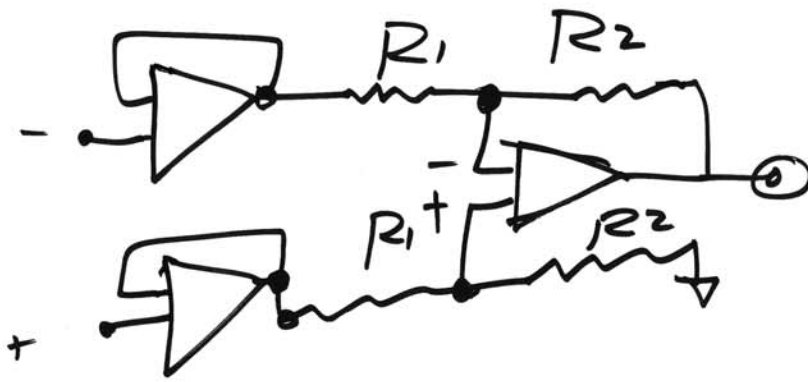

PER THE LM102 Data Sheet....

# REALLY GOOD CIRCUIT !!!

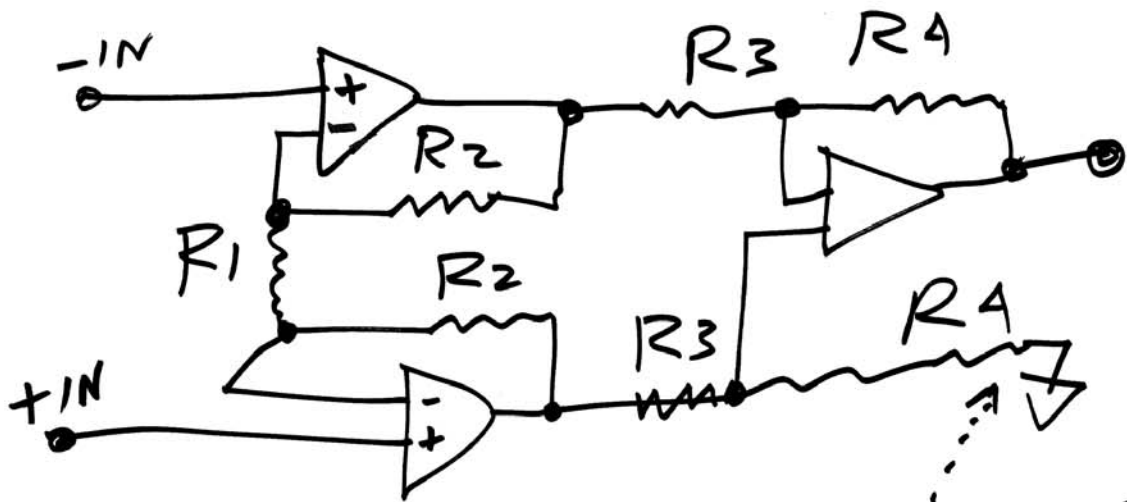

- BETTER GAIN
- BETTER BW.
- BETTER CMRR.....


-  $G = (R_2 + R_2/R_1) + 1 \times (R_4/R_3)$

- CMRR is improved

by  $R_4/R_3$

- BW is improved

# OTHER TRIM GAMES...

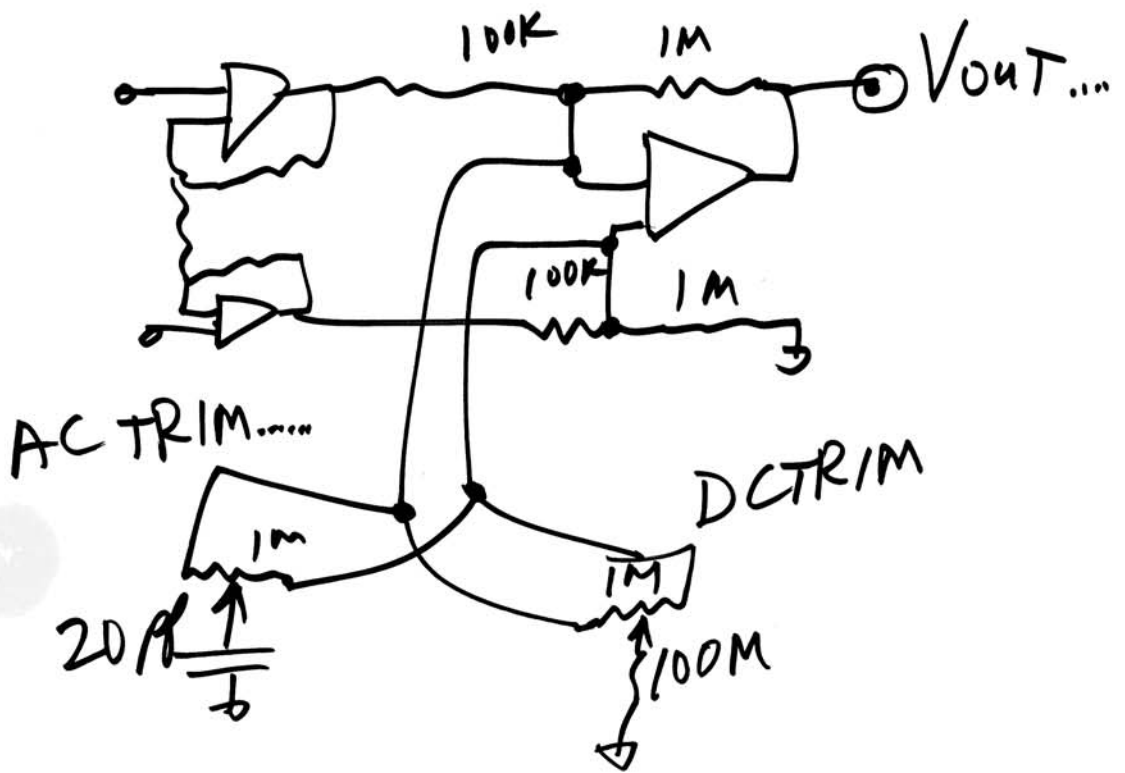




CAUTION ABOUT

C.M. SLEW  
RATE .....


SIMPLER IS BETTER

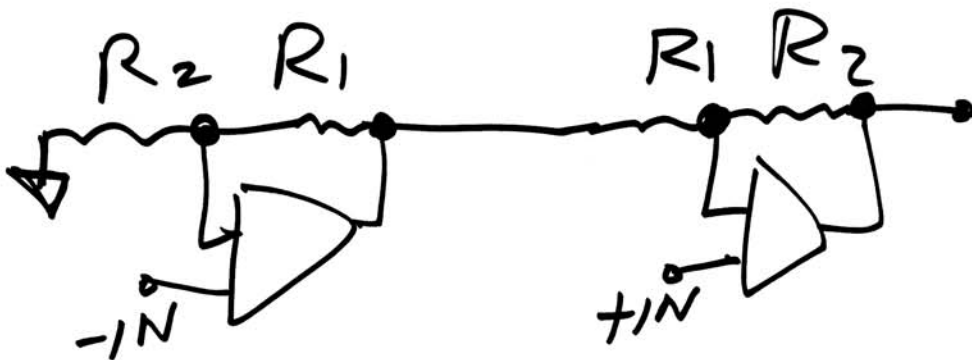

$$G = \frac{R_2}{R_1} + 1 !$$


(well, maybe NOT....)

GOOD NEWS!

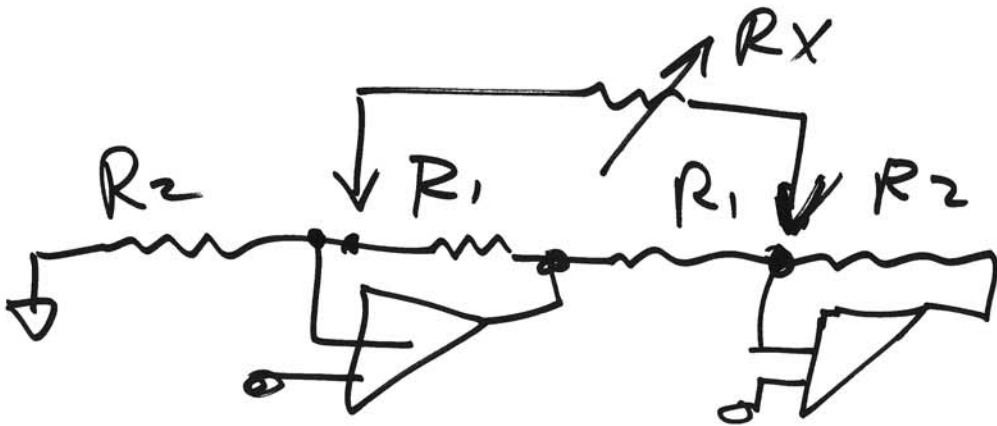


$$G = \left( \frac{R_2}{R_1} + 1 \right) + \left[ \frac{2R_2}{R_X} \right]$$

NOT SO GOOD NEWS...

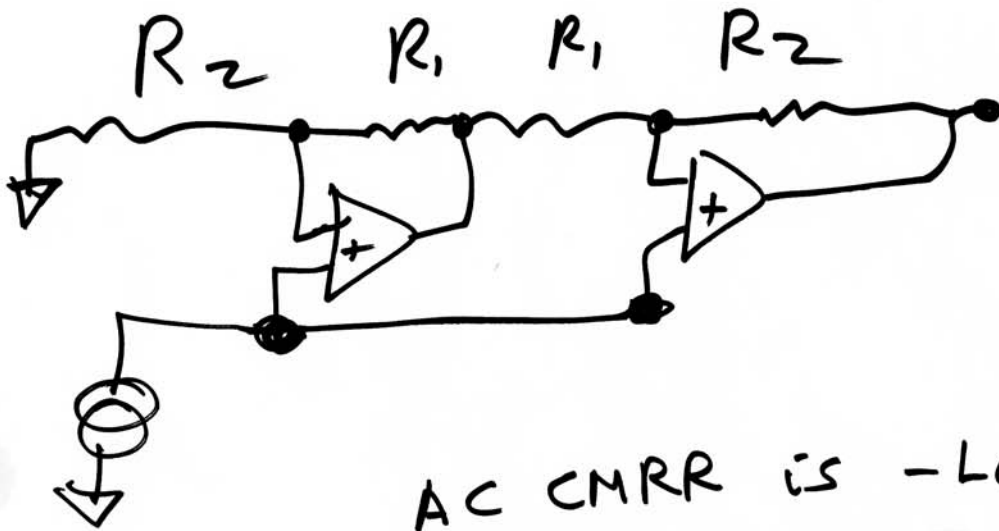


AC CMRR is -LOUSY....


GOOD  
BAND-AID  
TO  
COMPENSATE

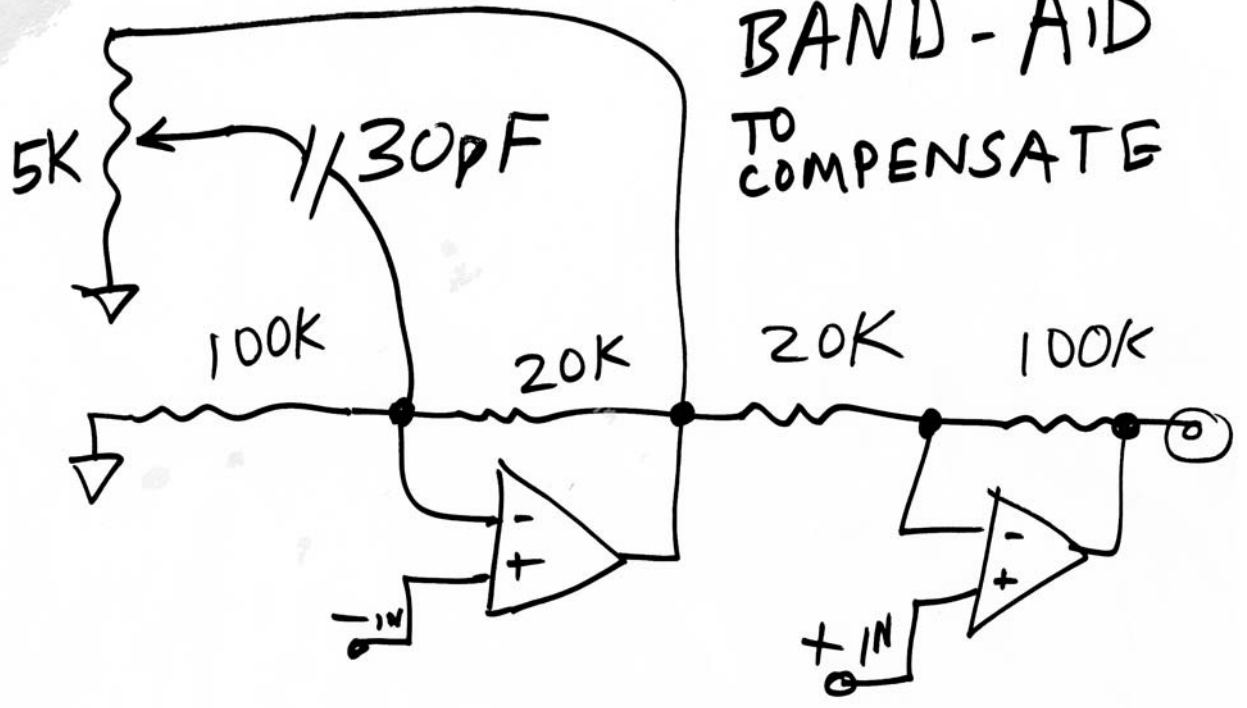

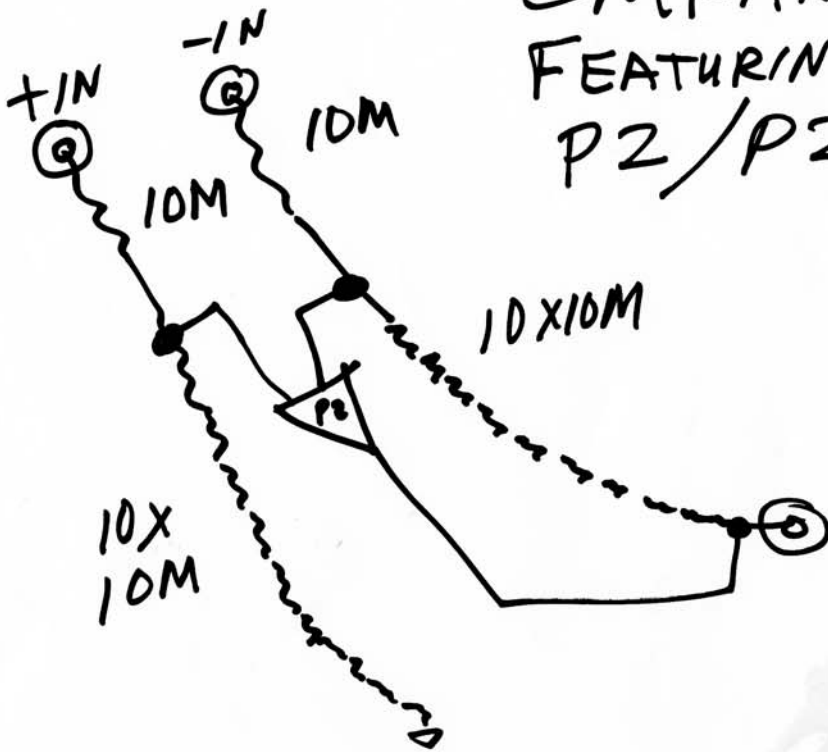$\pm 200$  VOLTS of  
CMRANGE  
FEATURING  
P2/P2A


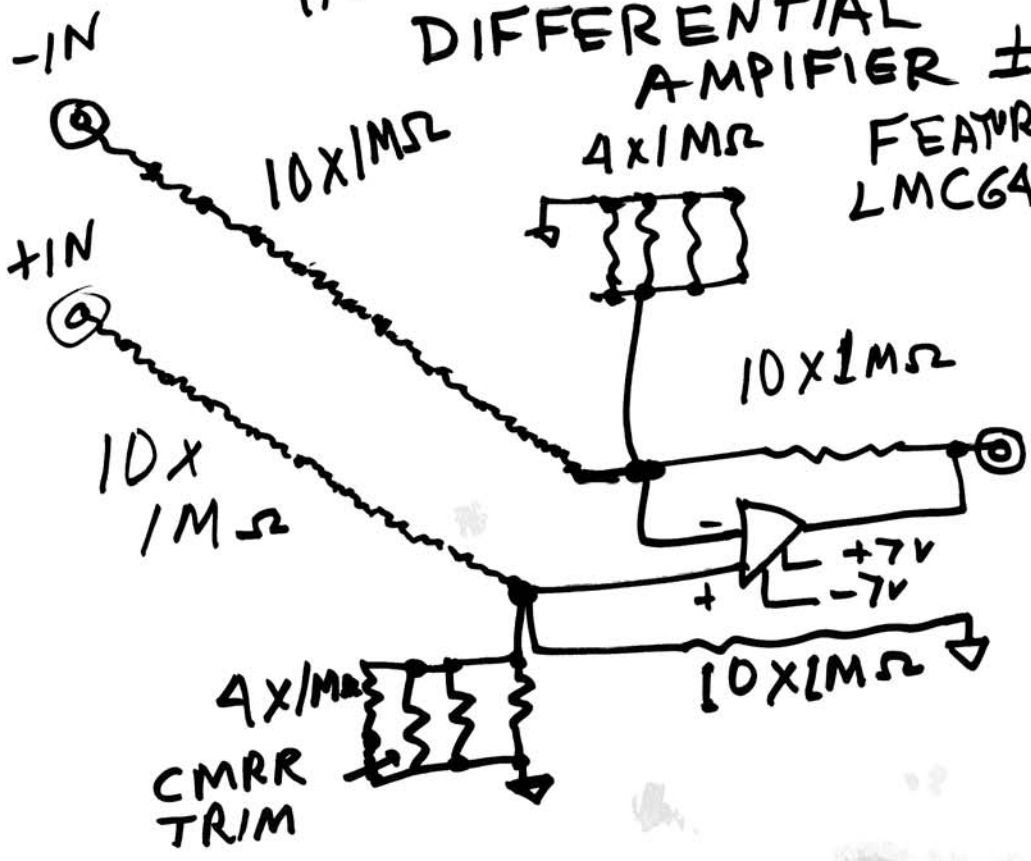
# HIGH CM-RANGE DIFFERENTIAL AMPLIFIER $\pm 200V$ FEATURING LMC6484



# DOUBLE INPUTS

LMH 6645, -46 -47 - (55MHz)  
LM 6152, 6154 (75MHz)  
LM 7301 (TINY)  
LM 6134, LM 6132 (LOW Power)  
LM 6142, 44 " "  
LM 8261, -62 - ( $\infty$  Cap Load)  
LM V931, -32, -34 (1.8V Supply)



# SMOOTH & SWOOPING

LMC 6482, -84

DUAL/QUAD

LMV 710, -711, -712

LOW PWR.

LMC 6462, -64

LOW POWER

LMC 8101

SINGLE

LMC 6494

QUAD

WHAT'S ALL THIS STUFF, ?

RAP 2005



**National Semiconductor provides a comprehensive set of support services. Product information, including sales literature and technical assistance is available through National's Customer Support Centers.**

### Americas

Email: [new.feedback@nsc.com](mailto:new.feedback@nsc.com)  
Phone: 1-800-272-9959

### Europe

Fax: +49 (0) 180-530 85 86  
Email: [europesupport@nsc.com](mailto:europesupport@nsc.com)  
Phone: Deutsch +49 (0) 69 9508 6208  
English +44 (0) 870 24 0 2171  
Français +33 (0) 1 41 91 87 90

### Asia Pacific

Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

### Japan

Fax: 81-3-5639-7507  
Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)  
Phone: 81-3-5639-7560



### The Bob Pease Show

All-analog talk show hosted by Bob Pease and streamed 24/7 from the National website.

[www.national.com/bobpeaseshow](http://www.national.com/bobpeaseshow)



### Analog University®

Expand your knowledge and understanding of analog with our free online educational training tool.

[analogU.national.com](http://analogU.national.com)